

① $R_1 = 100 \text{ ohms}$ $R_2 = 500 \text{ ohms}$

Joseph HATT
CSE ~~2020~~
3100-01/02

② $R_1 + R_2 = 100 + 500 = 600 \text{ ohms}$

In Series




$$R_1 + R_2$$

$$100 + 500$$

$$= 600 \text{ ohms}$$

③ In Parallel

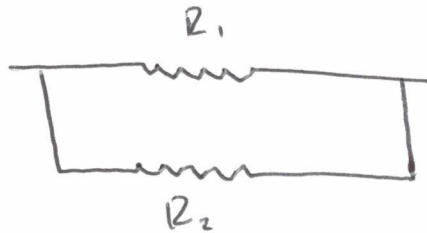


$$\frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{100} + \frac{1}{500} = \frac{6}{500}$$

$$= \frac{500}{6}$$


$$= 83.33 \text{ ohms}$$

4)

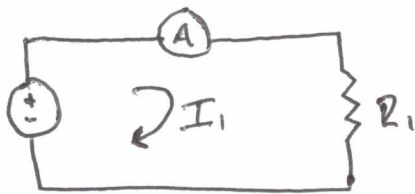

The internal resistance of an multimeter is ϕ .
This means it is short circuited.

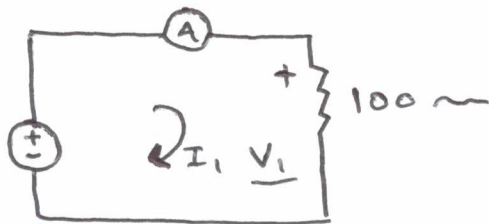A multimeter is used for calculating current and can act like an ammeter.



A ammeter is used to measure current



KVL: The sum of all potential drops in a loop is equal to zero.

As current is entering into the negative terminal of 5V. Negative convention is used.

$$-5 + V_1 = 0$$

$$(V = IR)$$

$$V_1 = I_1 \times 100$$


$$V_1 = 5$$

$$V_1 = \frac{5}{100}$$


$$= 5 \times 10^{-2}$$

$$A = 50 \times 10^{-3} A$$

$$I_1 = 50 mA$$

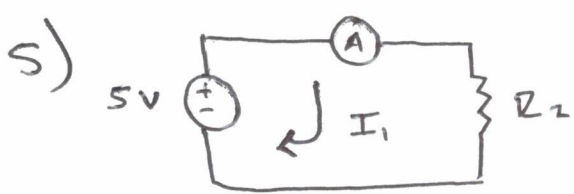

Multimeter is short circuited.

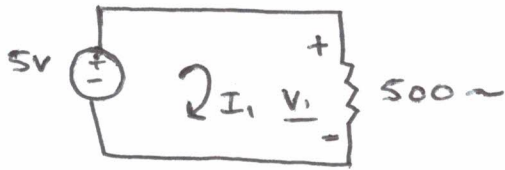

KVL: The sum of all potential drops in a loop is equal to zero.

Current is entering into a positive terminal of 500Ω and negative terminal of $5V$. So positive sign for V_1 and a negative sign ϕ for 5

$$-5 + V_1 = 0$$

$$V_1 = 5$$

V_1 (drop across 500Ω)

$$V_1 = 500 \times I_1$$

$$5 = 500 \times I_1$$


$$I_1 = \frac{5}{500} = 100$$

$$I_1 = \frac{1}{100}$$

$$= 1 \times 10^{-2}$$

$$= 10 \times 10^{-3} A$$


$$= 10 mA$$

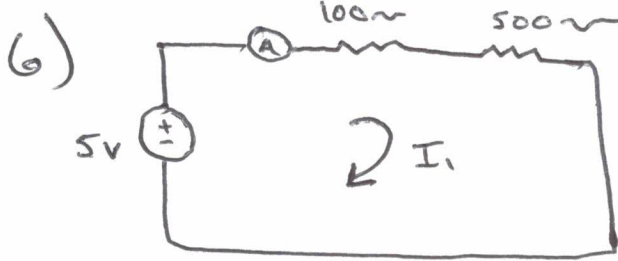

Ammeter is short circuited
 100Ω and 500Ω are in a
 series equivalent series
 resistance = $R_1 + R_2$

$$= 100 + 500$$

$$= 600\Omega$$

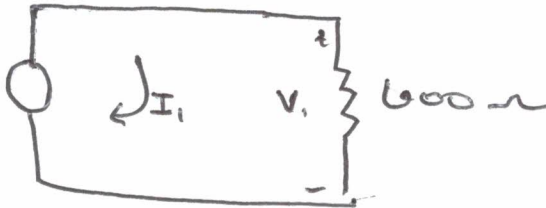

Positive sign for V_1 and
 negative sign for 5

$$-5 + V_1 = 0$$

$$V_1 = 5$$

$$V_1 = I_1 \times 600$$


$$I_1 = \frac{5}{600}$$

$$= \frac{5}{6} \times 10^{-2}$$

$$= 0.833 \times 10^{-2}$$

$$= 8.33 \times 10^{-3} \text{ A}$$

$$= 8.33 \text{ mA}$$

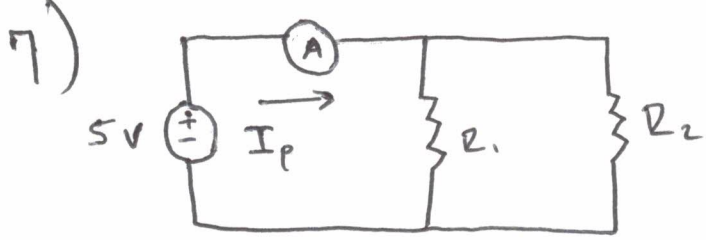


Ammeter is short circuited.
 R_1 and R_2 are in parallel

Equivalent parallel
 resistance = $\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$
 $= \frac{R_1 R_2}{R_1 + R_2}$
 $= \frac{100 \times 500}{600}$

$$R_{eq} = \frac{500}{6}$$

$$R_{eq} = 83.33 \Omega$$

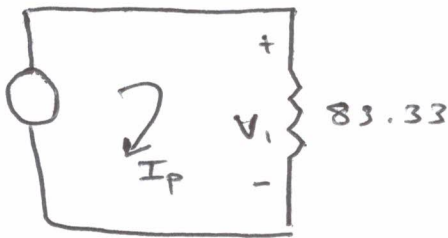

Positive sign for V_1 and negative sign for 5

$$-5 + V_1 = 0$$

$$V_1 = 5$$

$$V_1 = I_p \times 83.33$$

$$I_p = \frac{5}{83.33}$$

$$= \frac{15 \times 6}{100}$$

$$I_p = 6 \times 10^{-2} = 6 \times 10^{-3} A$$

$$I_p = 60 mA$$