

Lab 3

$$F(A,B,C,D) = A' B' C' D + CD + A C' D$$

1. Simplify F using K-map method.

CD \ AB		00	01	11	10
00	0	0	1	1	0
01	4	0	0	1	0
11	12	0	1	1	0
10	8	0	1	1	0

Handwritten annotations on the K-map:
 - A group of 1s in the first column (cells 0, 4, 12, 8) is labeled $AC'D$.
 - A group of 1s in the second column (cells 1, 5, 13, 9) is labeled $A'B'C'D$.
 - A group of 1s in the third column (cells 3, 7, 15, 11) is labeled CD .

Simplified k-map


CD \ AB		00	01	11	10
00	0	0	1	1	0
01	4	0	0	1	0
11	12	0	1	1	0
10	8	0	1	1	0

Handwritten annotations on the simplified K-map:
 - A group of 1s in the first column (cells 0, 4, 12, 8) is labeled AD .
 - A group of 1s in the second column (cells 1, 5, 13, 9) is labeled BD .
 - A group of 1s in the third column (cells 3, 7, 15, 11) is labeled CD .

The simplified of $F(A, B, C, D) = AD + B'D + CD$

2. Draw the logic diagram (with gates) of the simplified F function from part (1).

Simplified Circuit:

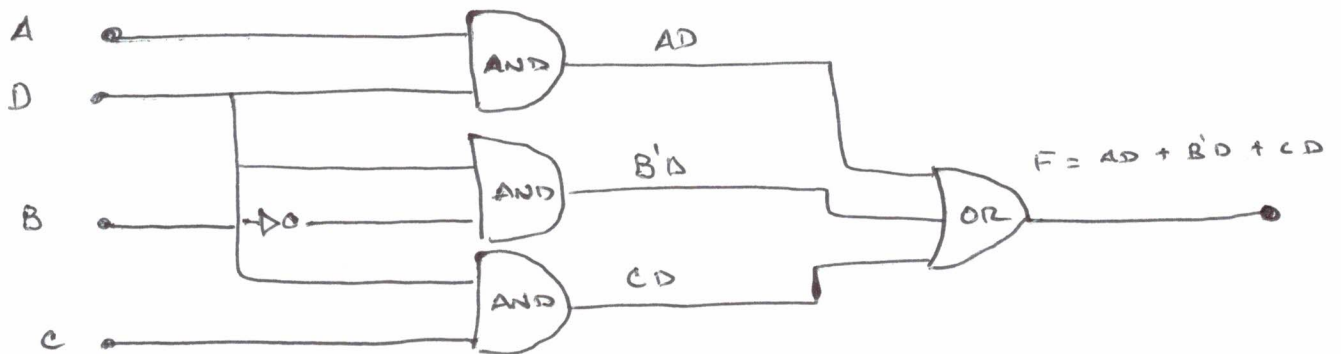

Explanation:


The negation of any logical identity P is nothing but opposite truth value for P. If P is T then (negation P) is F AND gate is used to find the product of two literals P AND gate Q output is PQ OR gate is used to find the sum of two literals P OR Gate Q output is P + Q.

3. Implement the logic diagram from part(2) with NAND gates.

Given $F(A, B, C, D) = AD + B'D + CD$

$$[F'] = [(AD + B'D + CD)']$$

$$F = [(AD)'(B'D)'(CD)']$$

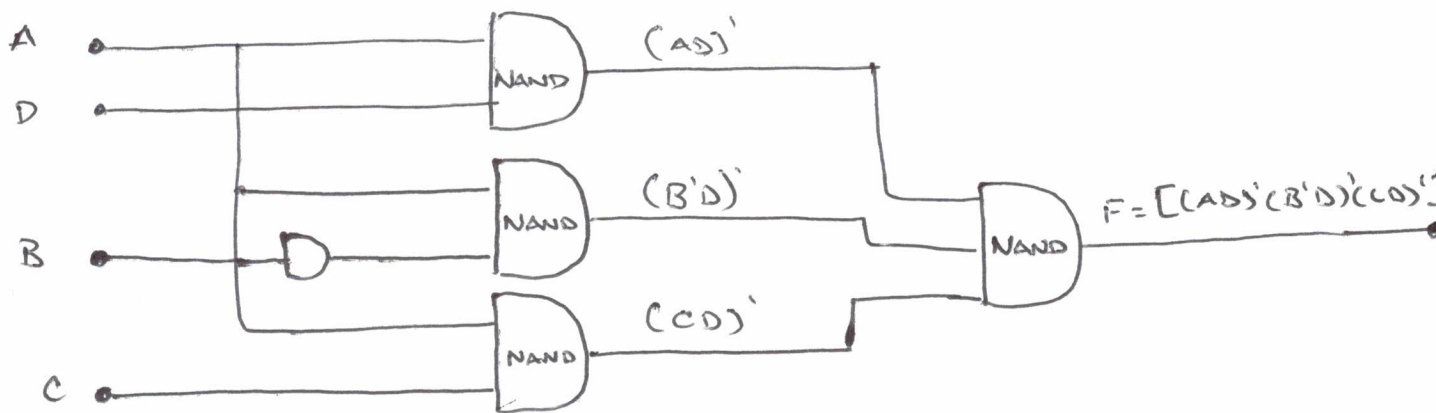

Explanation:

NAND gate is used to find the product of two literals P NAND gate Q output is $(PQ)'$.

4. Simplify the function F algebraically (you should get the same as the simplified function from part(1), please use proper algebraic rules to simplify).

$$F = A'B'C'D + CD + AC'D$$

$$F = A'B'C'D + AC'D + CD$$

$$F = C'D(A'B' + A) + CD \quad \text{(by distributive law } PQ + PR = P(Q+R))$$

$$F = C'D[(A' + A)(B' + A)] + CD \quad \left| \begin{array}{l} P + QR = (P+Q)(P+R) \\ P + P' = 1 \end{array} \right.$$

$$F = C'D[(1)(B' + A)] + CD$$

$$F = (B'C'D + AC'D) + CD \quad \left| \begin{array}{l} P(Q+R) = PQ + PR \\ PQ + PR = P(Q+R) \end{array} \right.$$

$$F = B'C'D + D(AC' + C) \quad \left| \begin{array}{l} P + QR = (P+Q)(P+R) \\ P + P' = 1 \end{array} \right.$$

$$F = B'C'D + D[(A + C)(C' + C)]$$

$$F = B'C'D + D[(A + C)(1)] \quad \left| \begin{array}{l} P + P' = 1 \\ P(Q+R) = PQ + PR \end{array} \right.$$

$$F = B'C'D + (AD + CD) \quad \left| \begin{array}{l} P(Q+R) = PQ + PR \end{array} \right.$$

$$F = B'C'D + CD + AD$$

$$F = D(B'C' + C) + AD \quad \left| \begin{array}{l} PQ + PR = P(Q+R) \end{array} \right.$$

$$F = D[(B' + C)(C' + C)] + AD \quad \left| \begin{array}{l} P + QR = (P+Q)(P+R) \\ P + P' = 1 \end{array} \right.$$

$$F = D[CB' + C](1) + AD$$

$$F = (B'D + CD) + AD \quad \left| \begin{array}{l} P(Q+R) = PQ + PR \end{array} \right.$$

$$F = AD + B'D + CD$$

which is the required simplified function from part 1